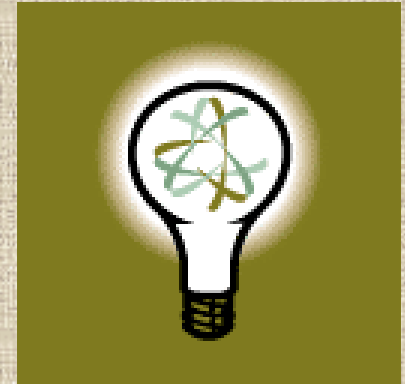



Electrical



Module 1



Basic Electrical Circuit

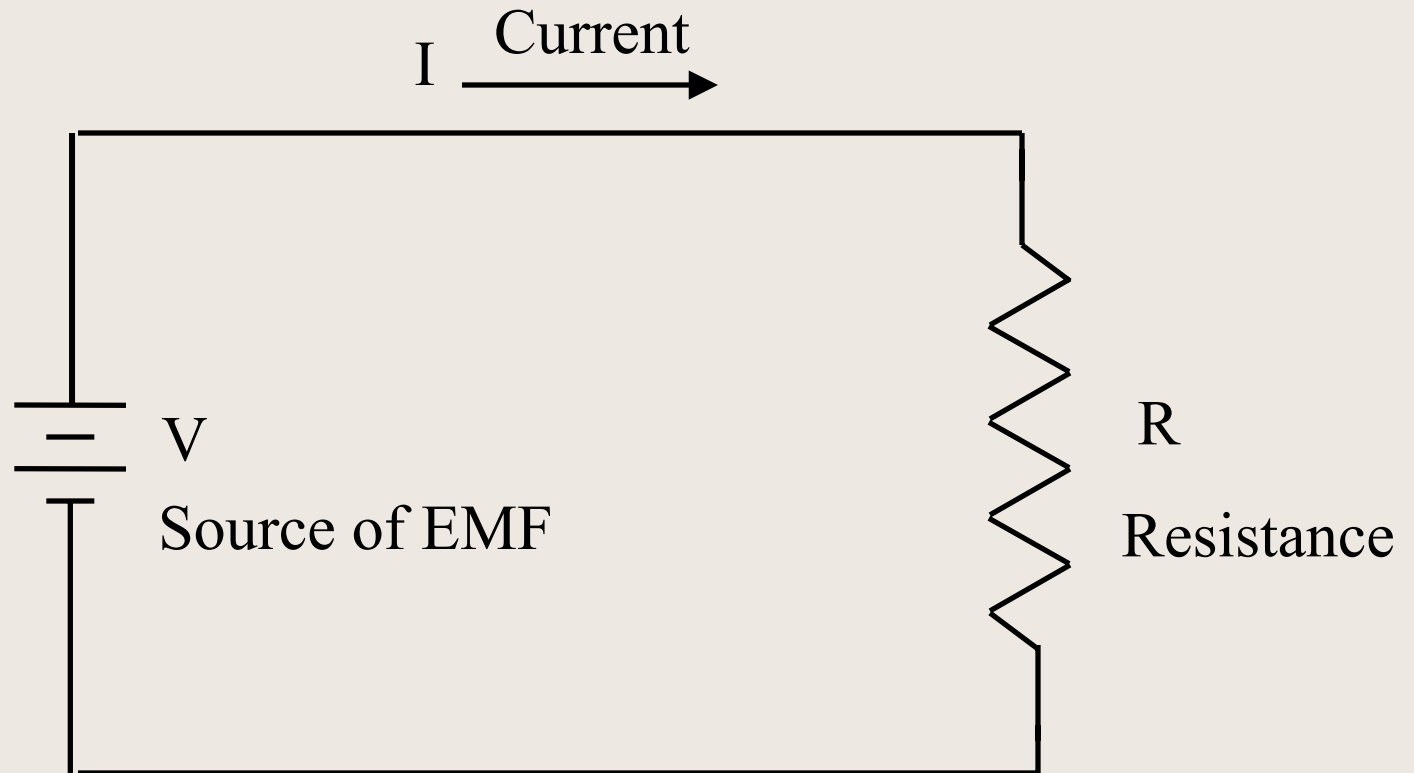


Basic Terms

- Current
- Voltage
- Resistance

Ohm's Law


$$I = \frac{V}{R}$$

Capacitors

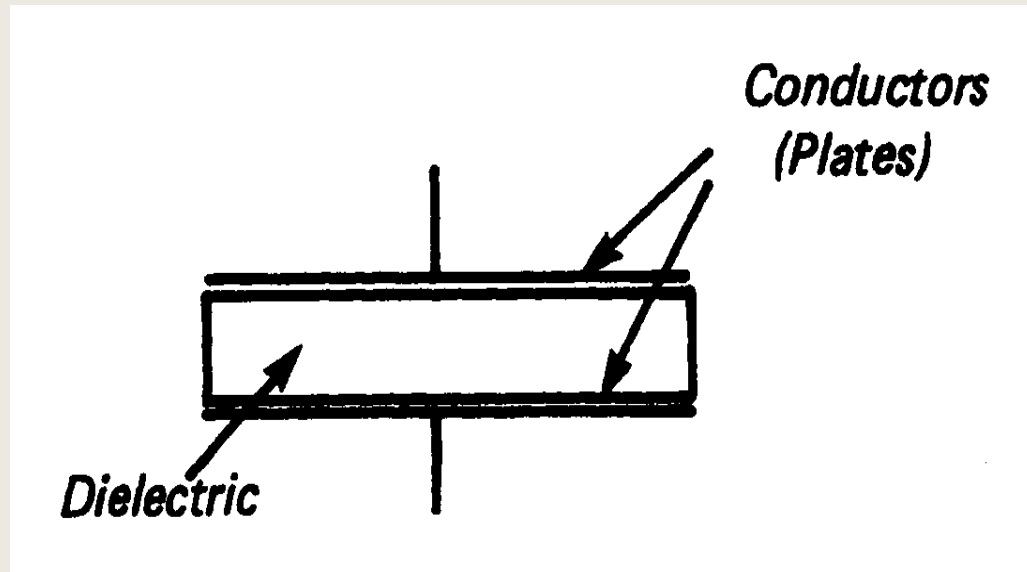


$$C = \varepsilon \frac{A}{d}$$

Magnetic Field

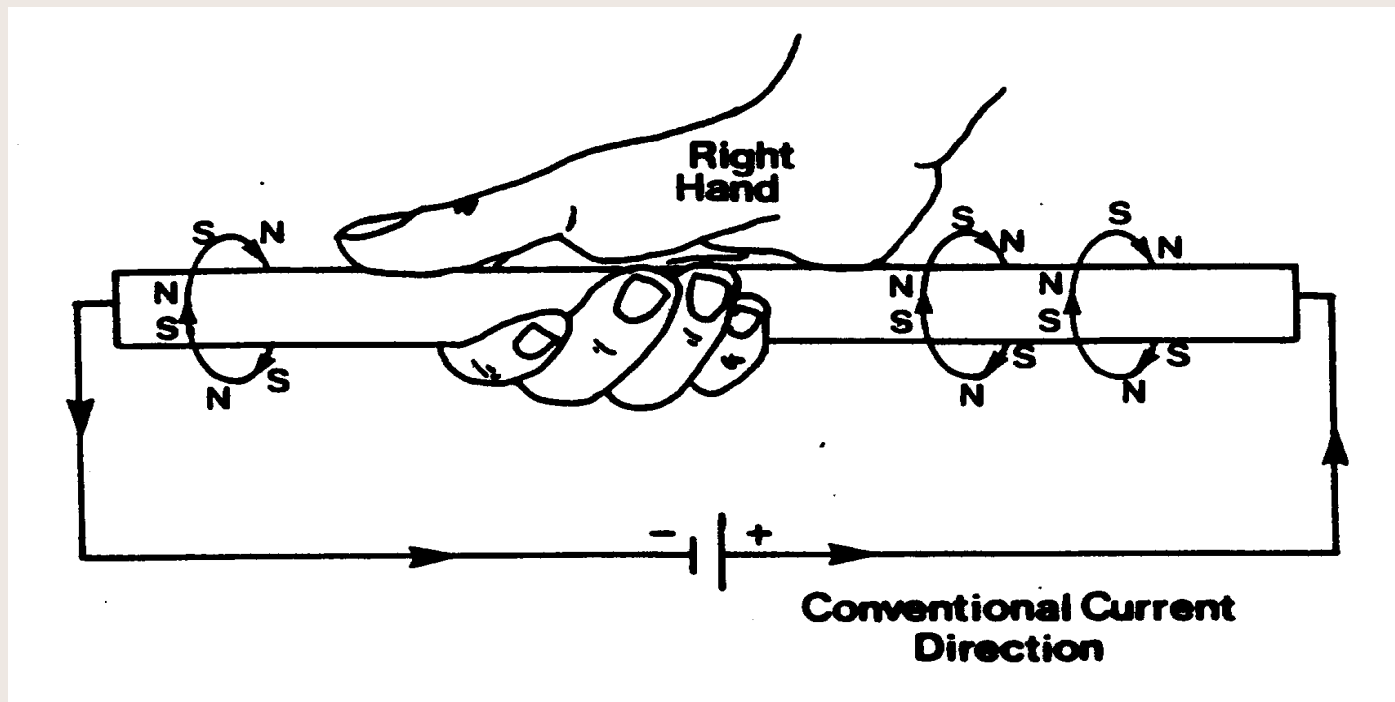

Coil

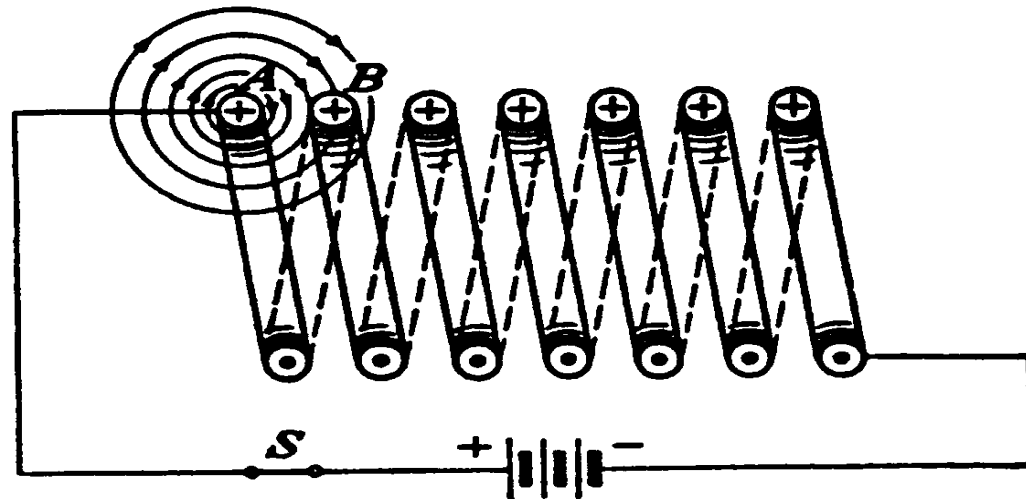

Inductors, Capacitors & ac

- Ac circuits have continuously changing values of voltage and current
- Inductors and capacitors continuously oppose these changes
- Opposition to current is called **reactance**
- Measured in ohms

$$X_L = 2\pi fL$$


$$X_C = \frac{1}{2\pi fC}$$

Reactance Voltages & Currents


$$V_{X_L} = I_{X_L} \times X_L$$

$$V_{X_C} = I_{X_C} \times X_C$$


Terminology

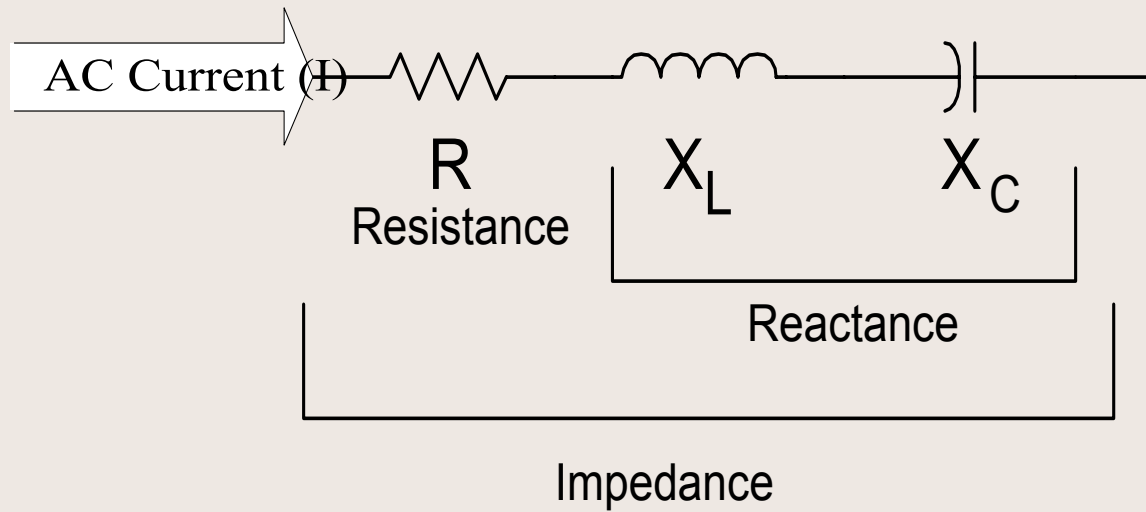

Resistors

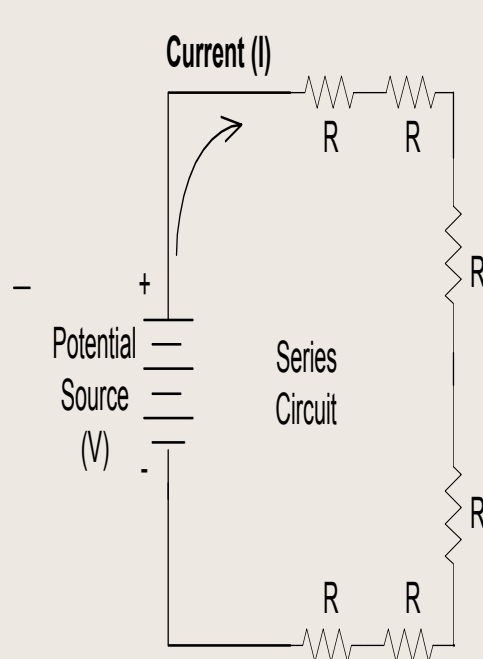


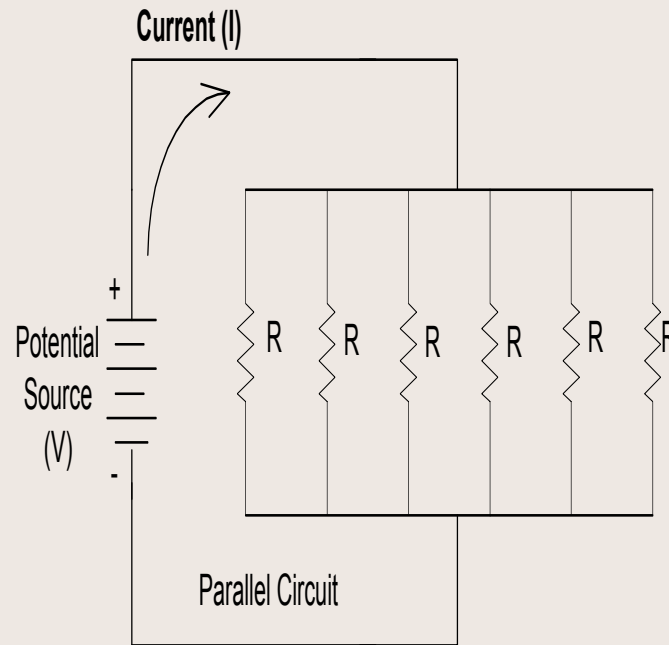With all 6 Resistances the same value (R)
Current would be 6 times less
that of 1 resistance (R)




With all 6 Resistances the same value (R)
Current would be 6 times more
that of 1 resistance (R)

Capacitor in a DC circuit

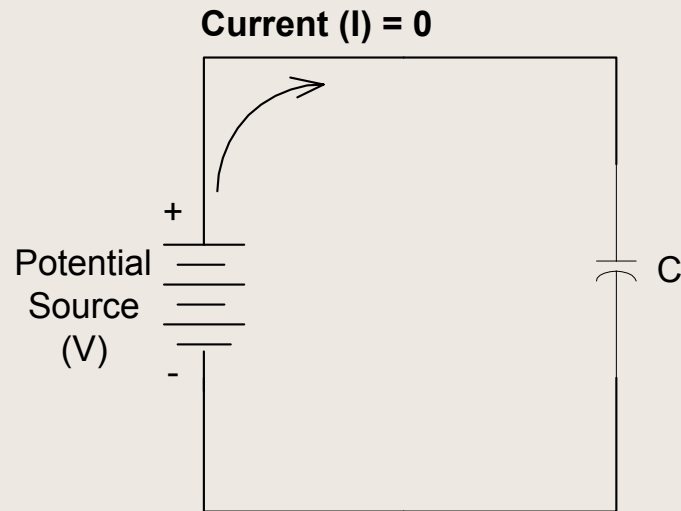


Capacitors will not pass DC Current

Capacitive Transients

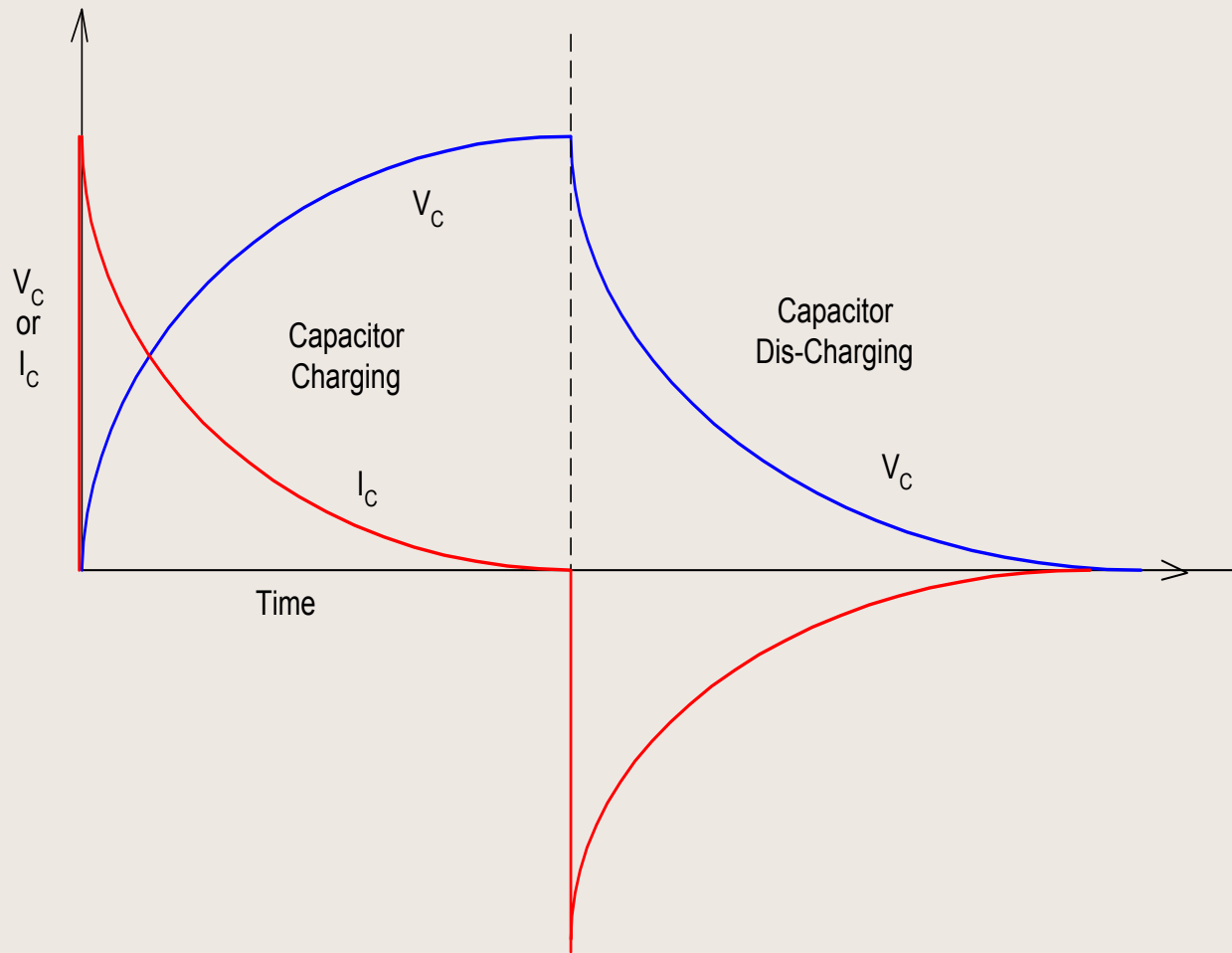


Inductor in a DC circuit

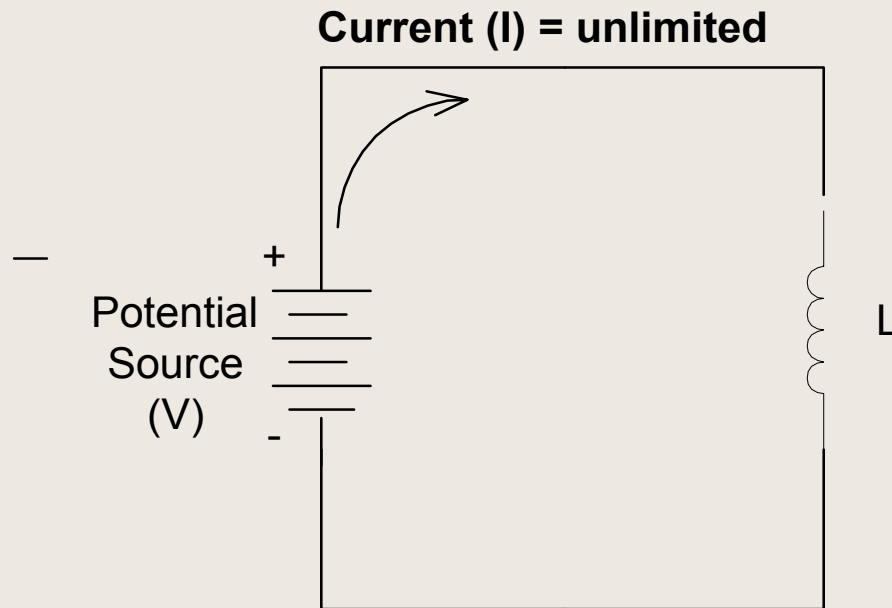


Inductors are a Short circuit to DC Current



Inductor Transients

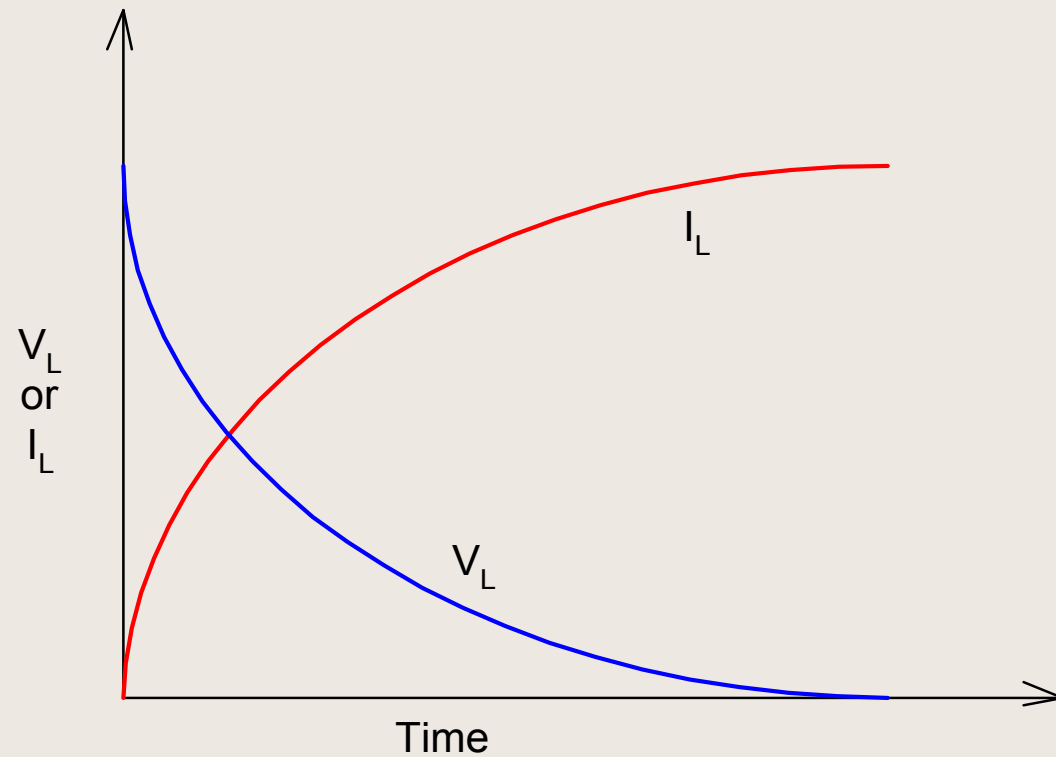

Sine curves and phasors


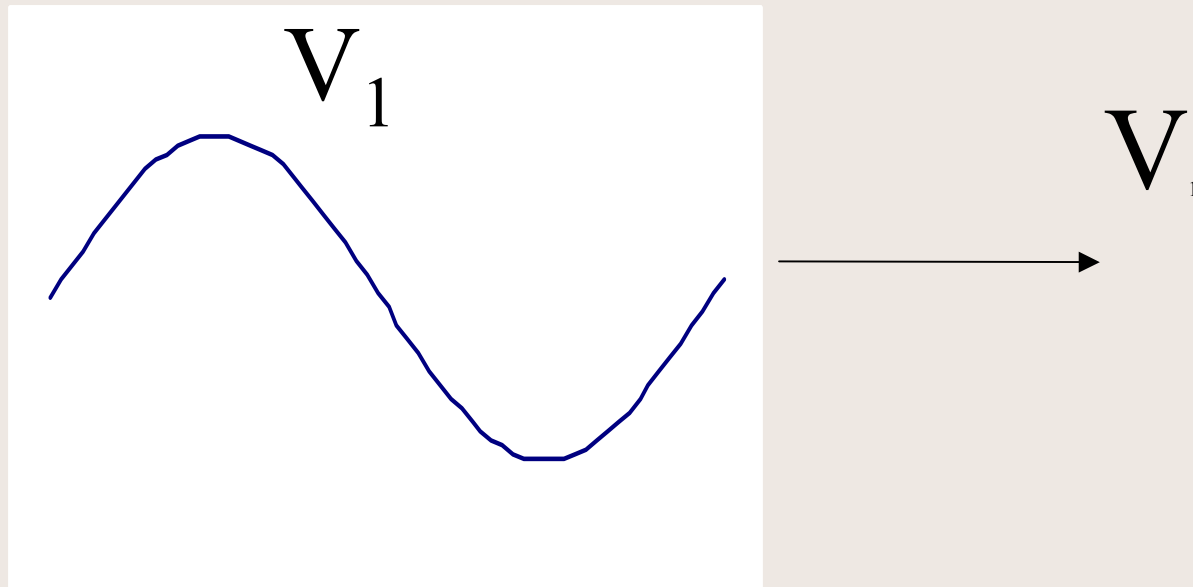


Phasor Diagram

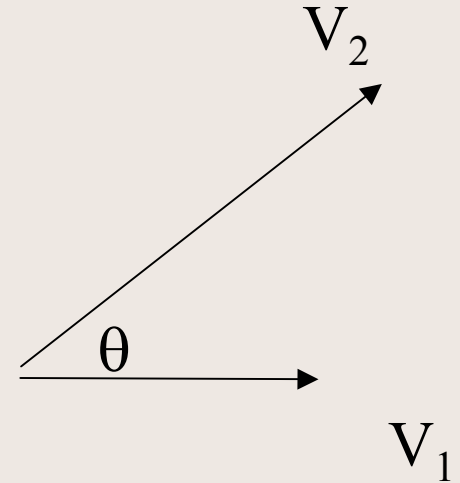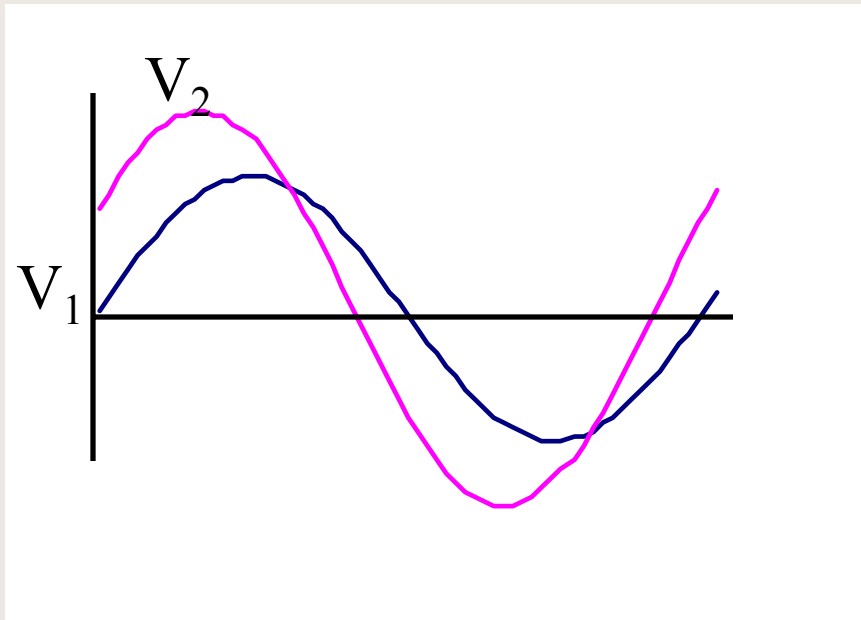


V_2 Leads V_1 by θ


Resistive Circuit

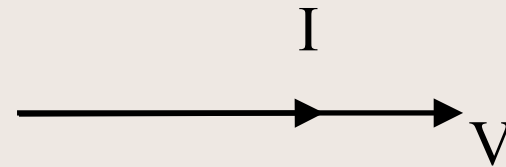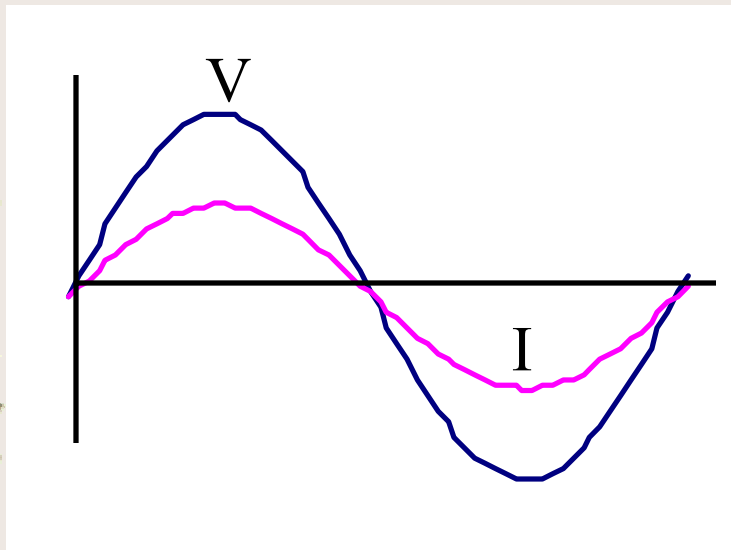

Series & Parallel Inductors

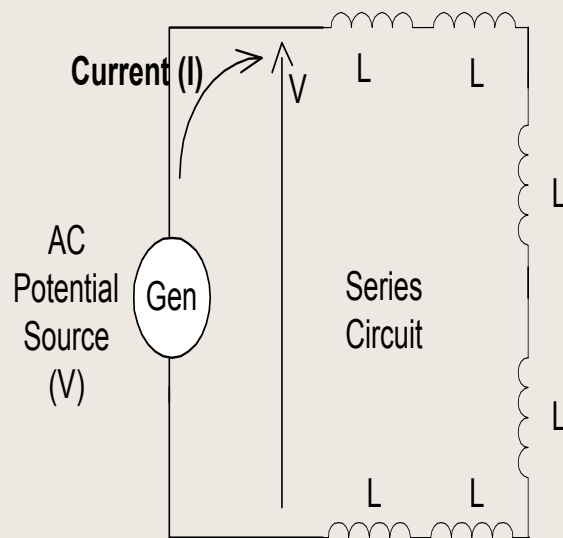


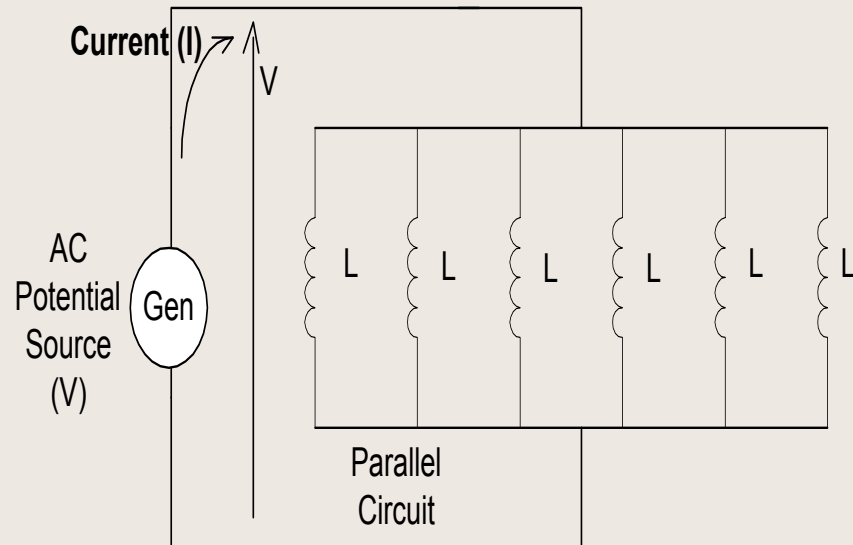
With all 6 Inductances the same value (L)
Current would be 6 times less
that of 1 Inductance (L)




With all 6 Inductances the same value (L)
Current would be 6 times more
that of 1 Inductance (L)

In both circuits the Current will lag the Voltage by 1/4 cycle

Inductive Phasors

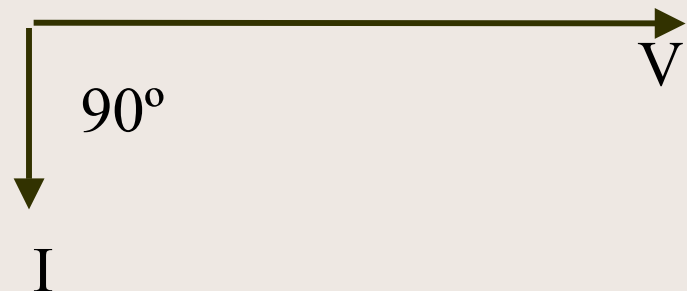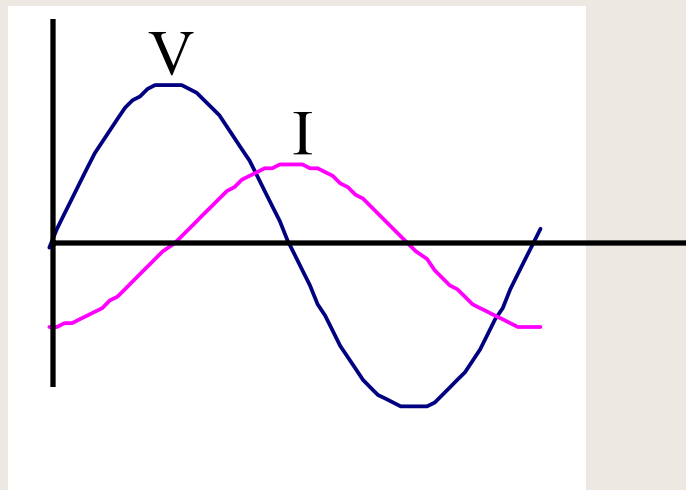

Series & Parallel Capacitors


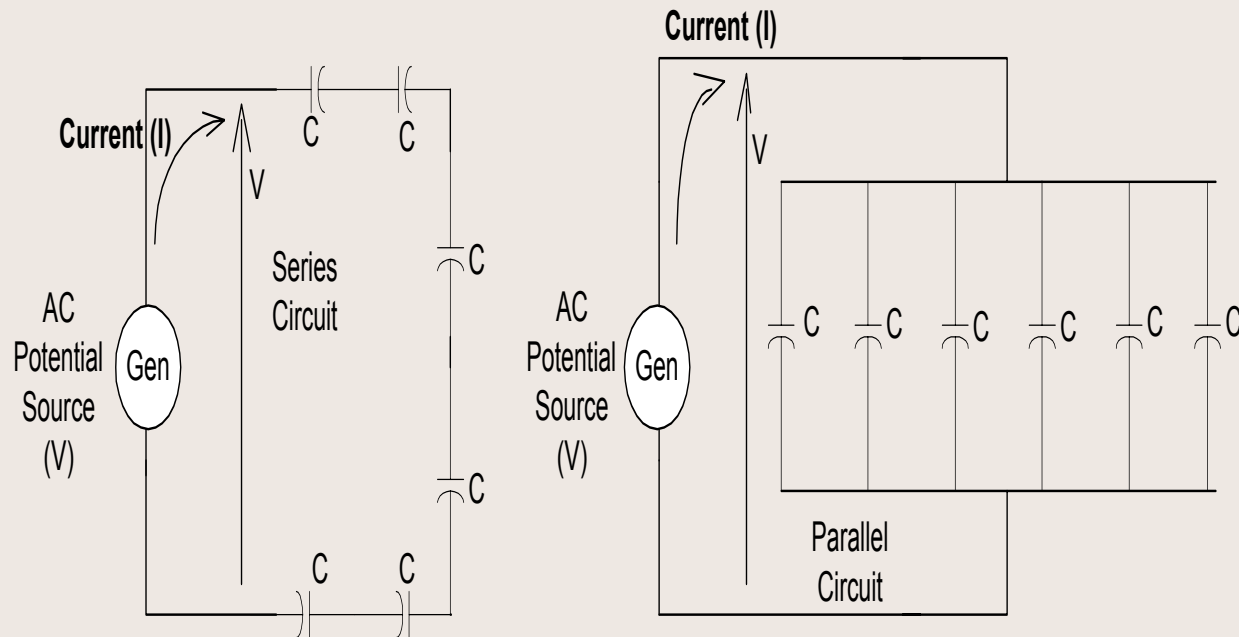


With all 6 Capacitances (C) the same value
Current would be 6 times less
that of 1 Capacitance


With all 6 Capacitances (C) the same value
Current would be 6 times more
that of 1 Capacitance

In both circuits the Current will lead the Voltage by 1/4 cycle


Capacitive Phasors

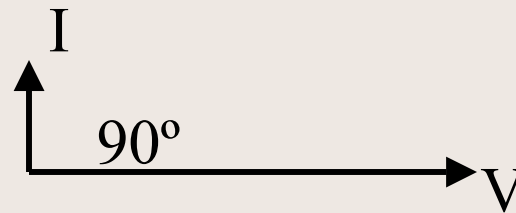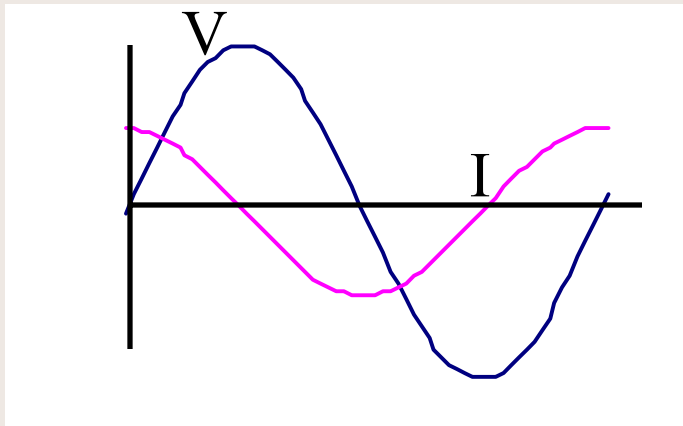


Phasors for a typical circuit

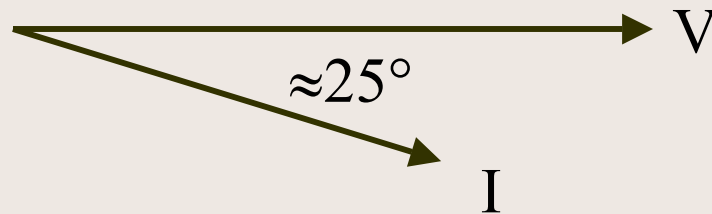

Resistor and Inductor in Series

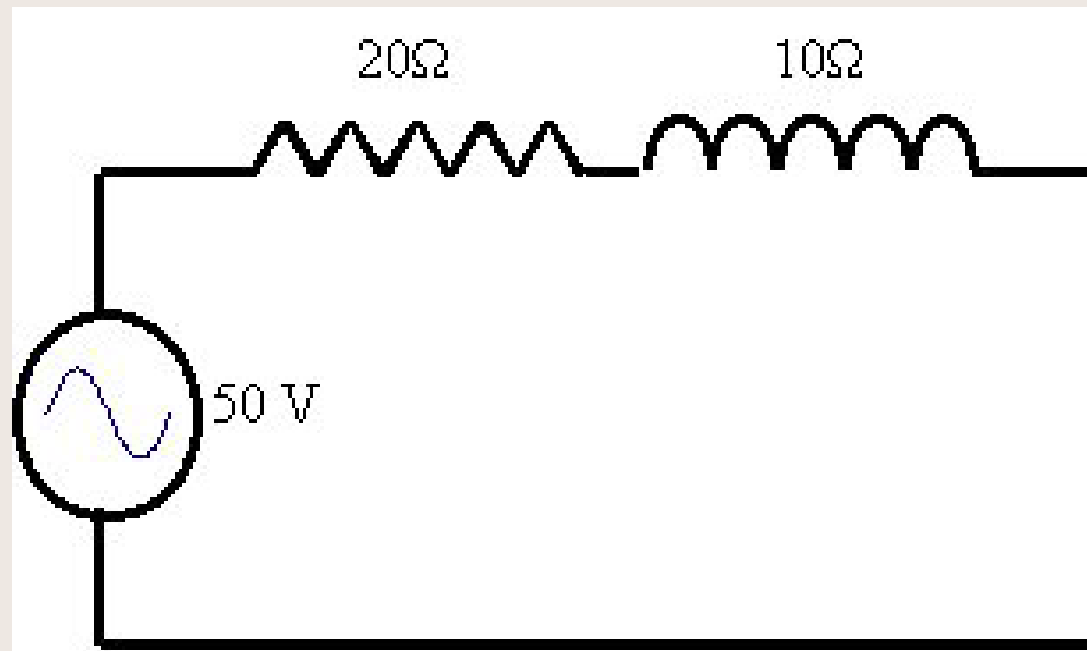

Impedance Triangle

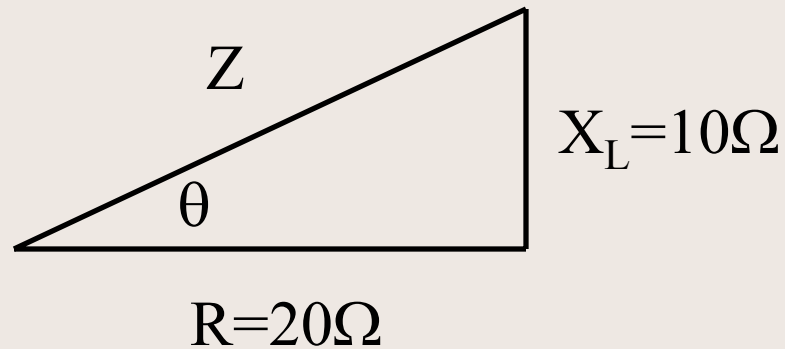


What is the impedance of the circuit?

What is the phase angle?


Acrostic

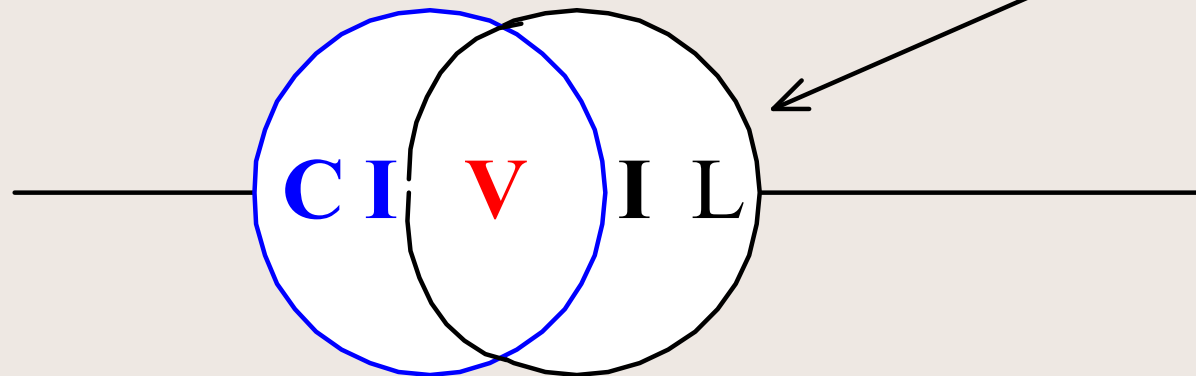V comes before (leads) **I** in an Inductor




I comes before (leads) **V** in a Capacitor


Power

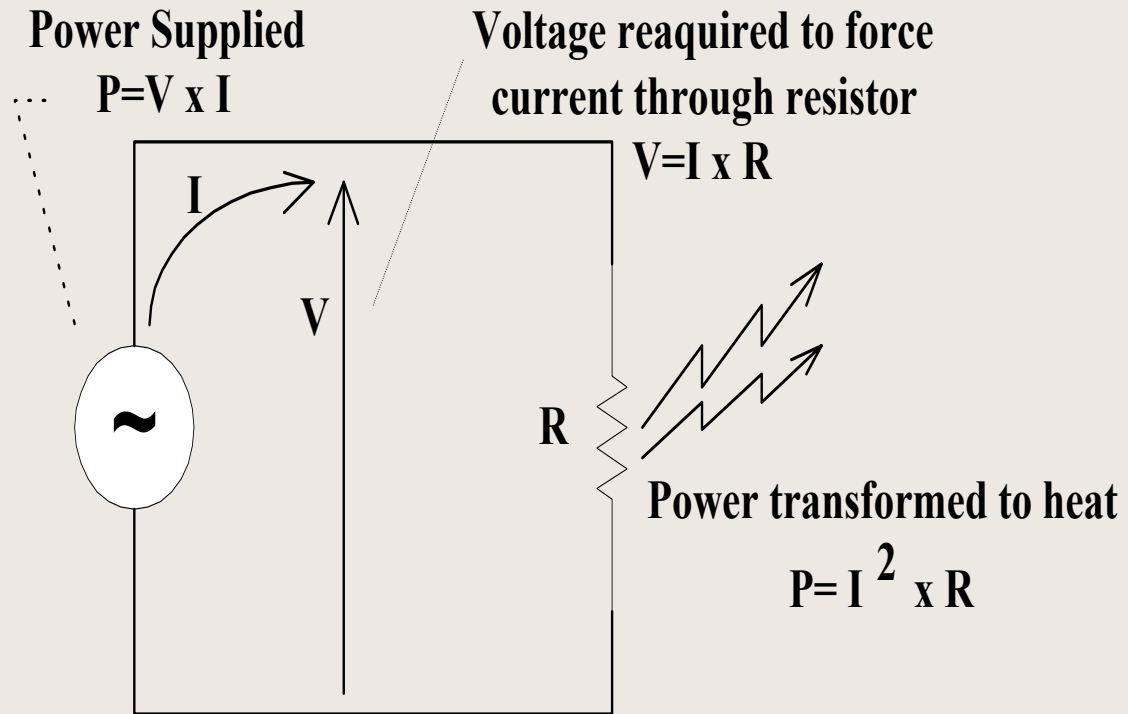


Power wave in a resistive circuit

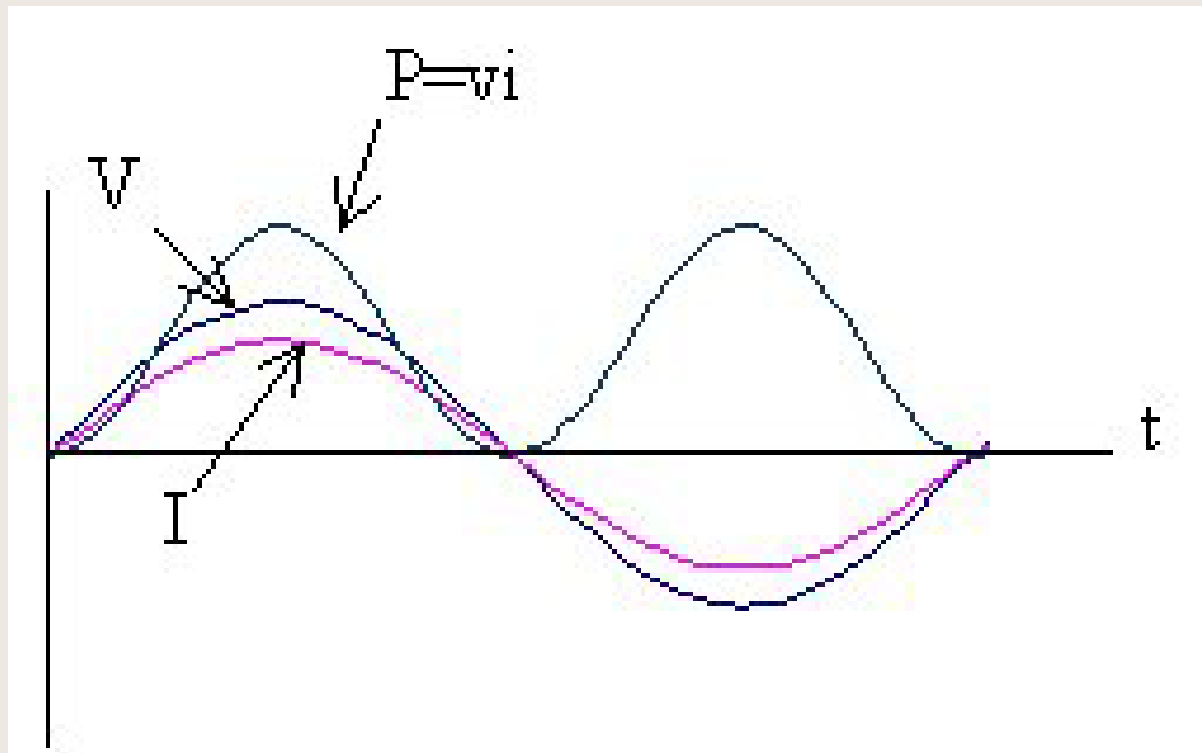


Power in a capacitive circuit

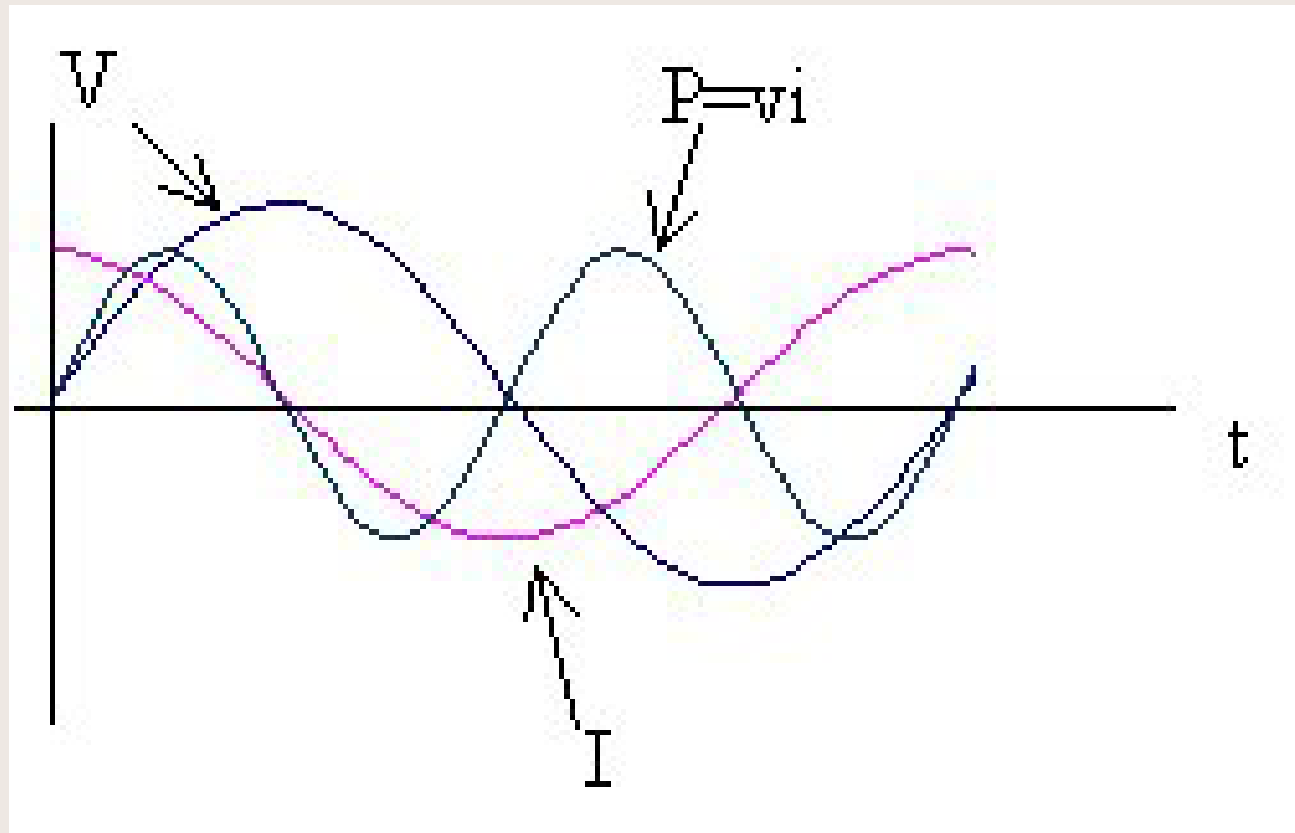


Power in an inductive circuit

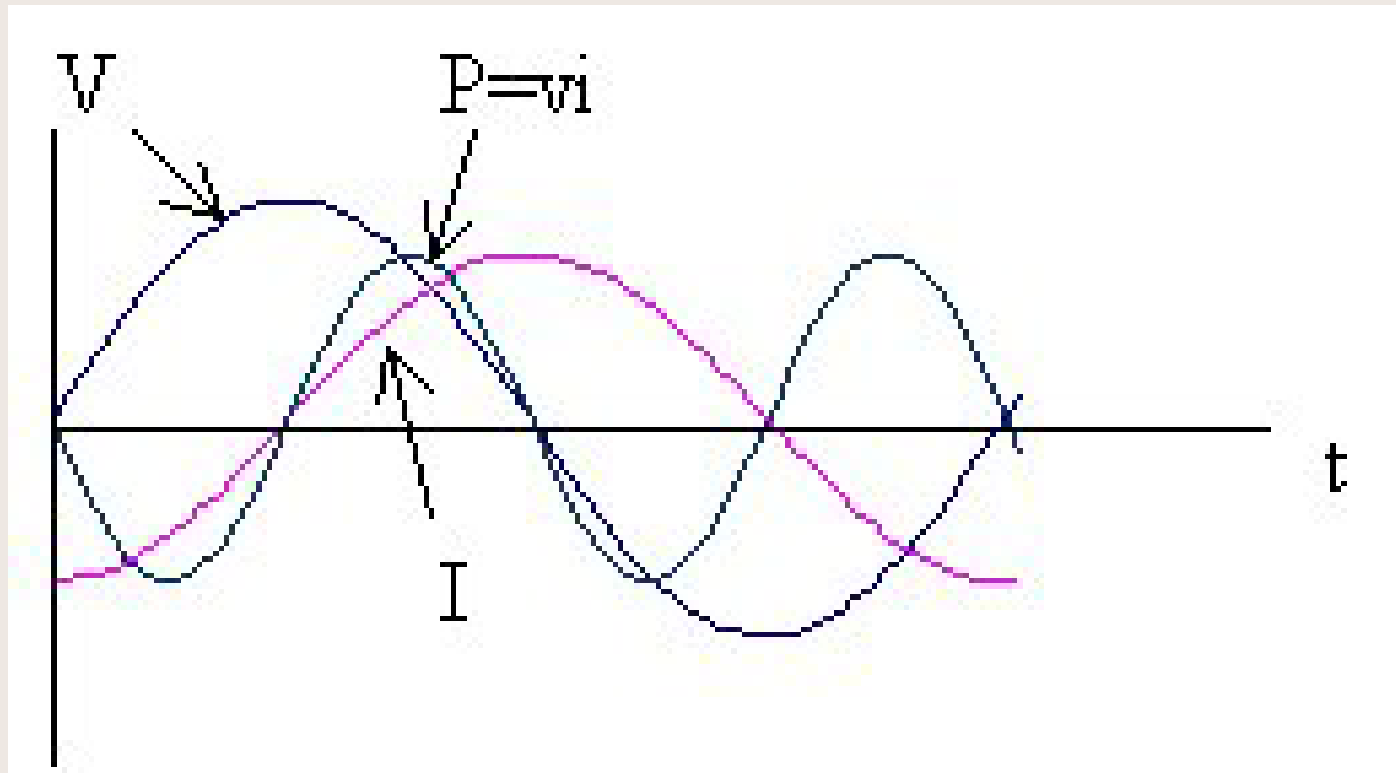


Power in a real circuit

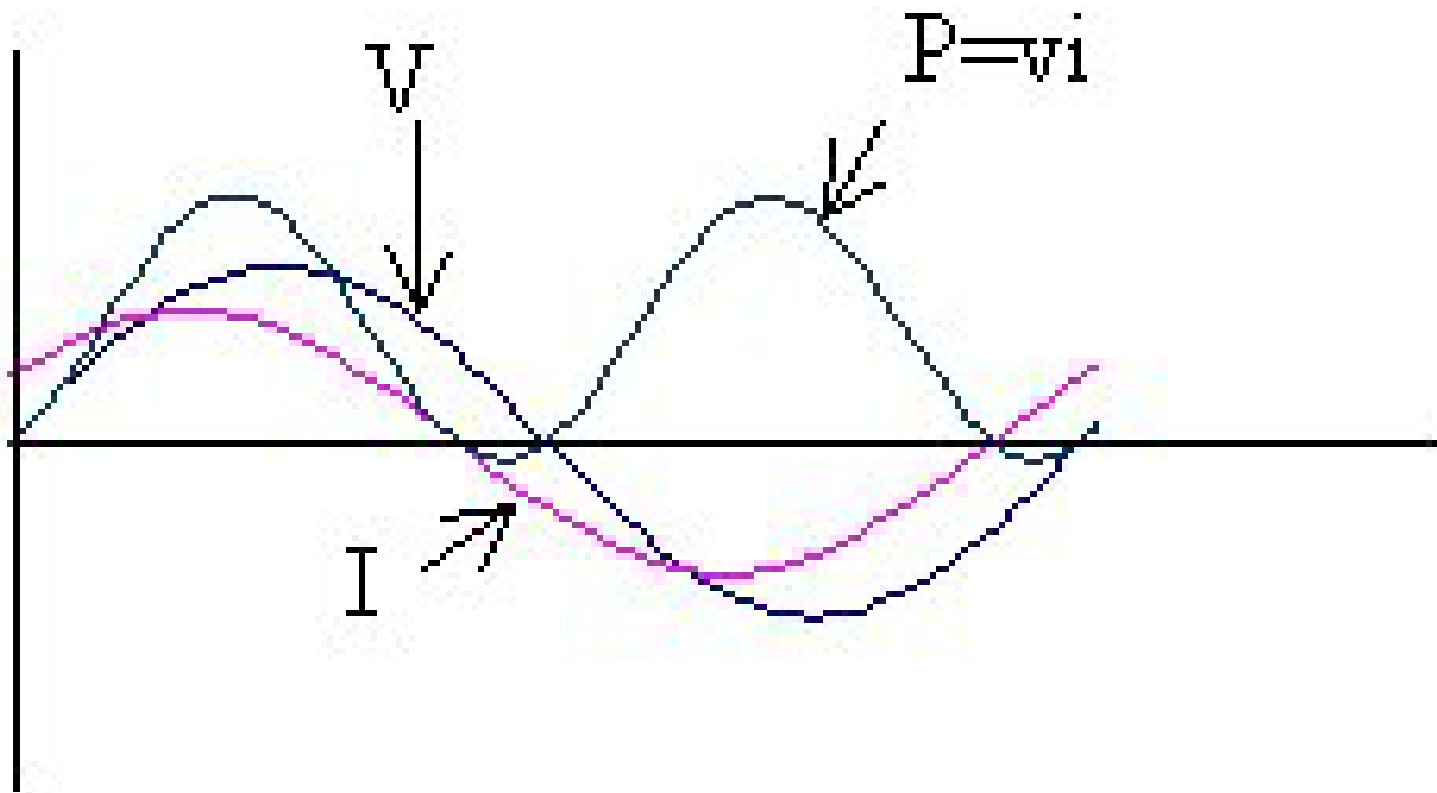


Power Triangle

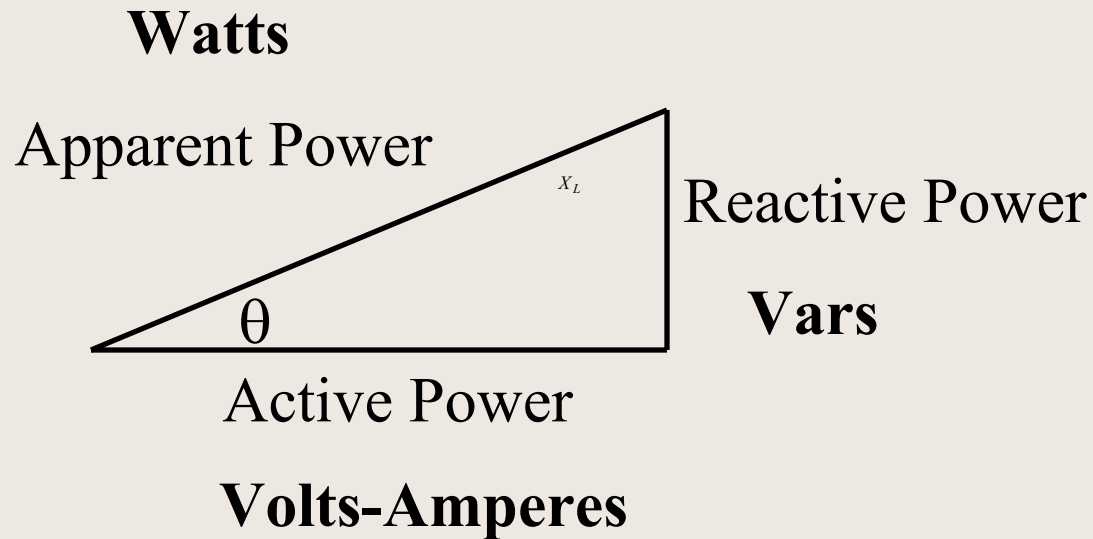


Direction of magnetic field

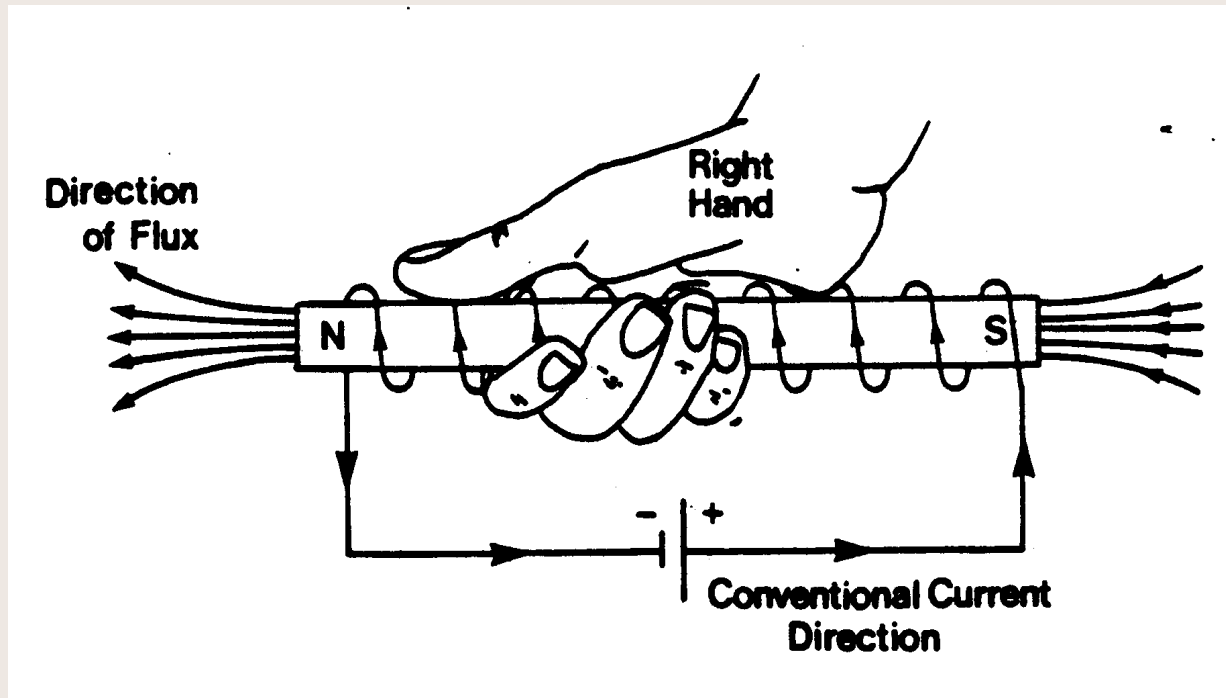


Motor Action

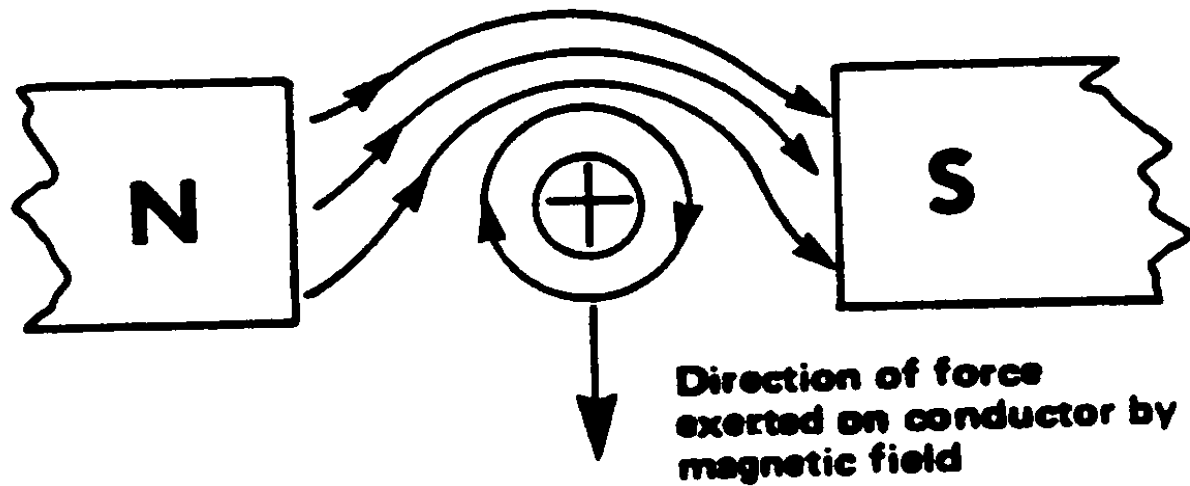


Electromagnetic Induction

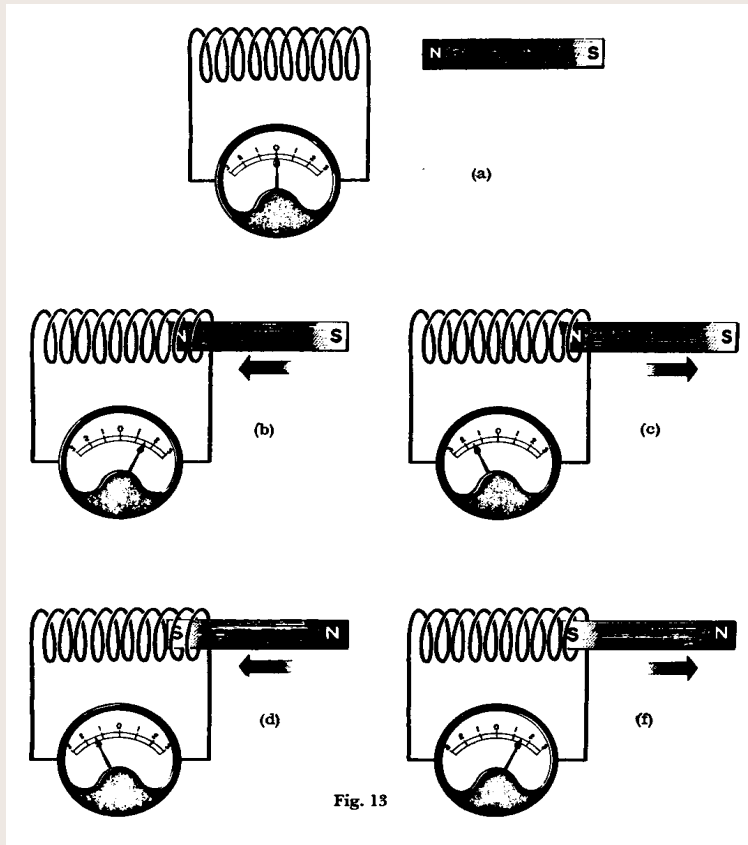


Transformer

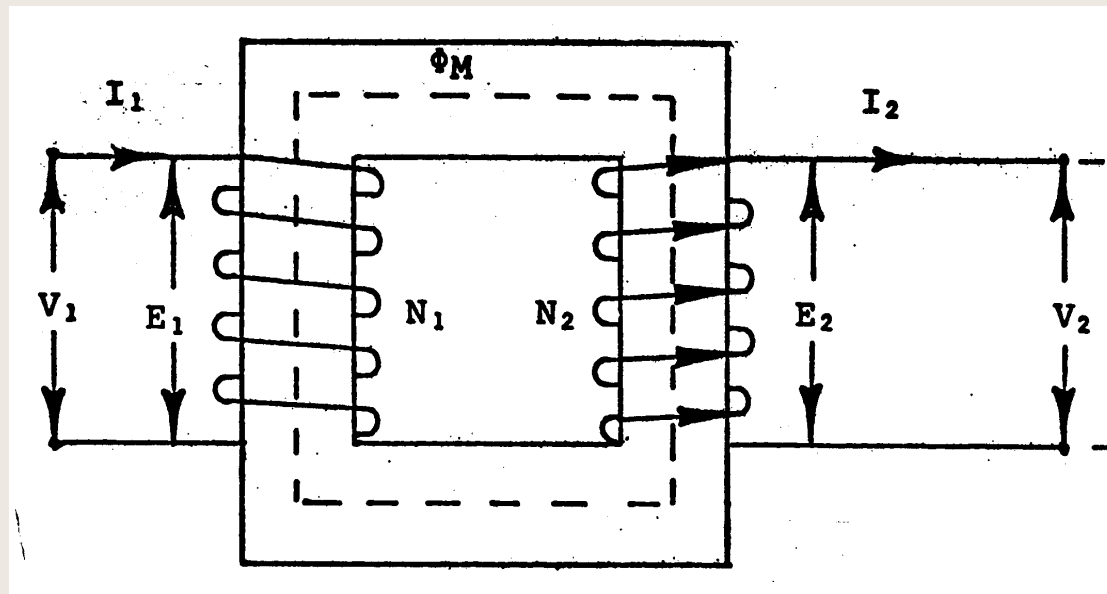


Motor

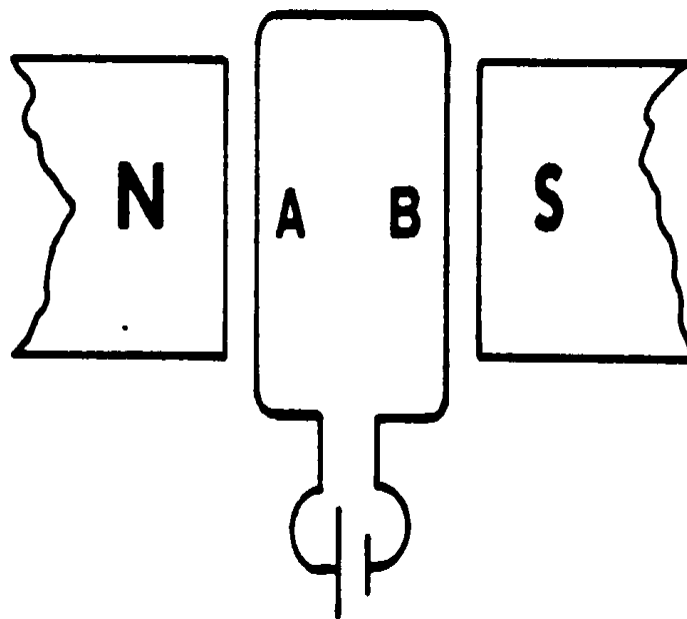


Motor

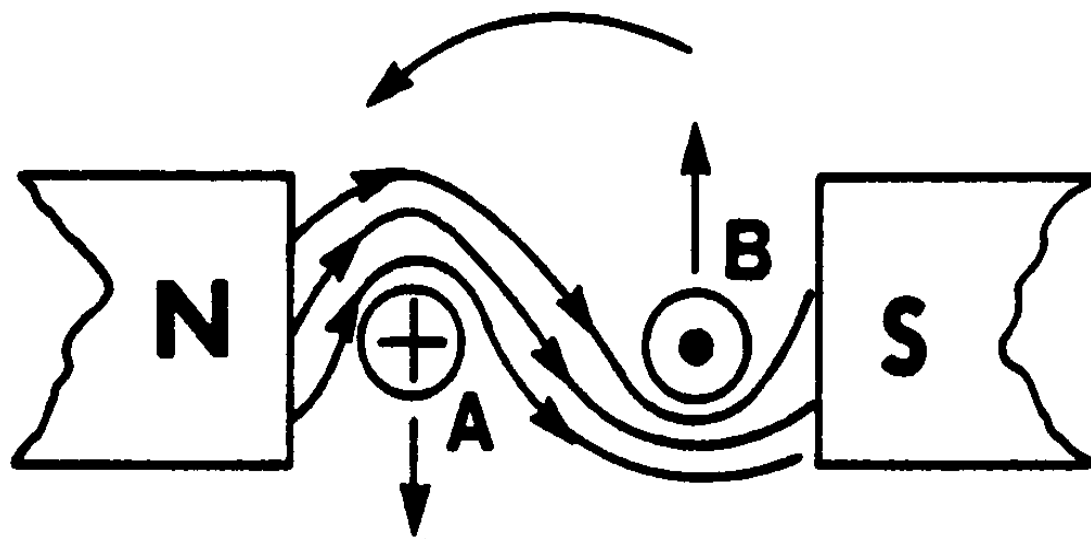






Series Motor

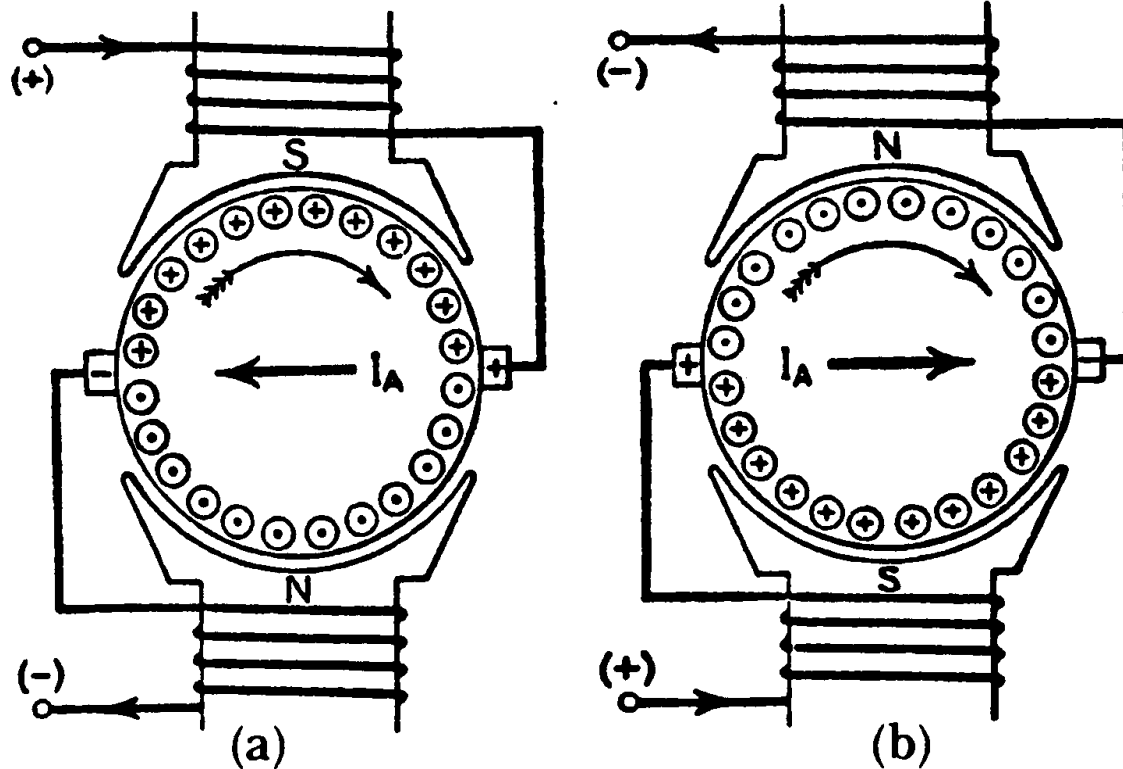



Basic Generator

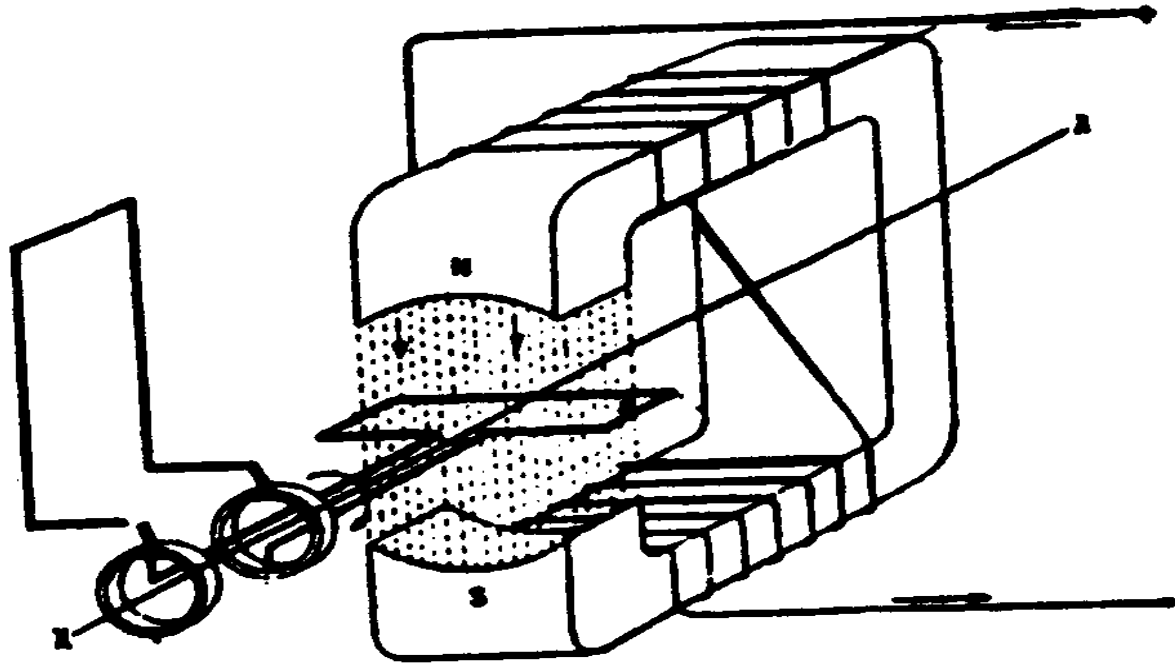


Generation of Sinusoidal Voltage

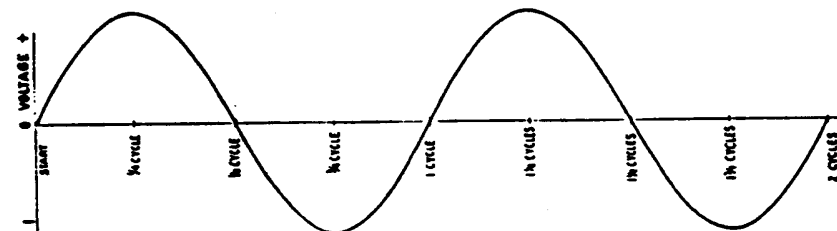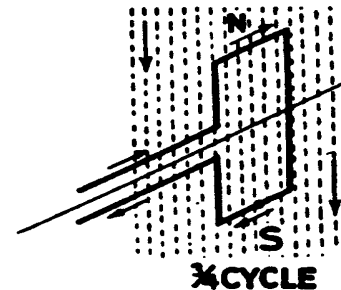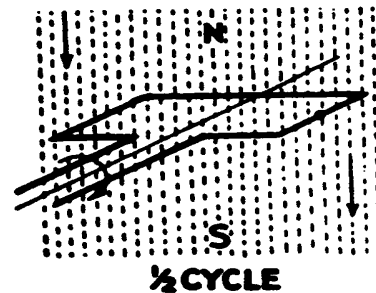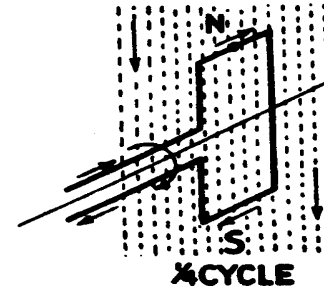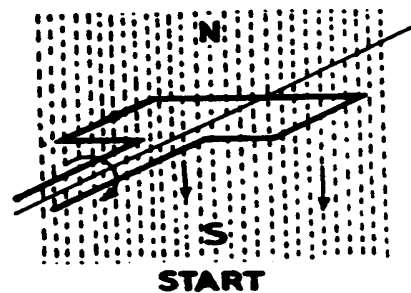

Spinning Magnet

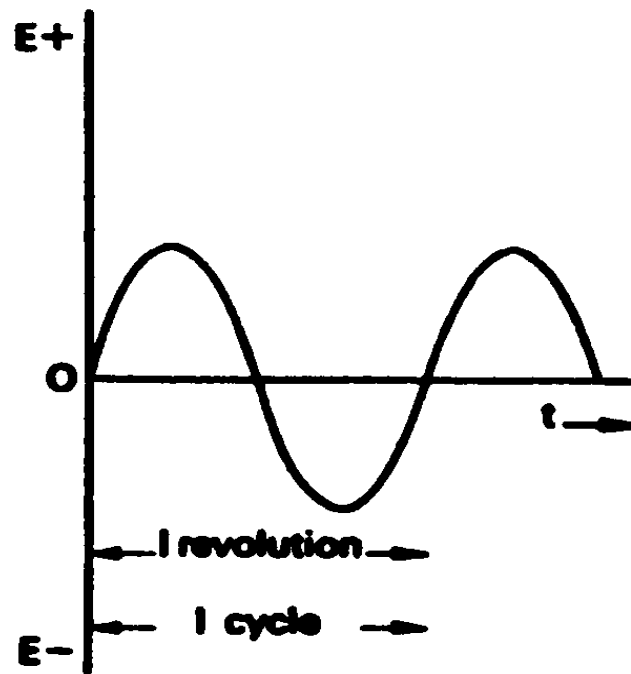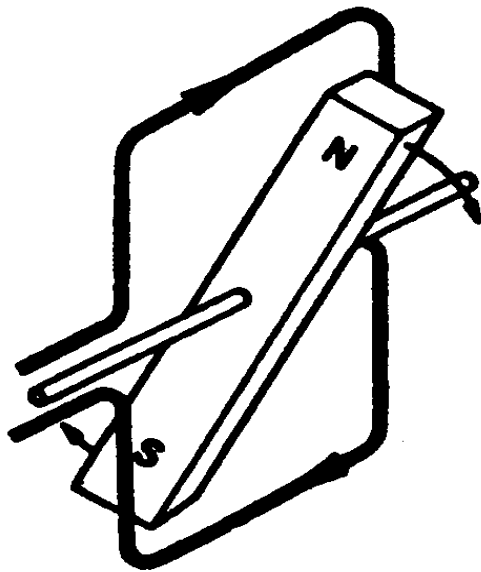


Three phase Generation

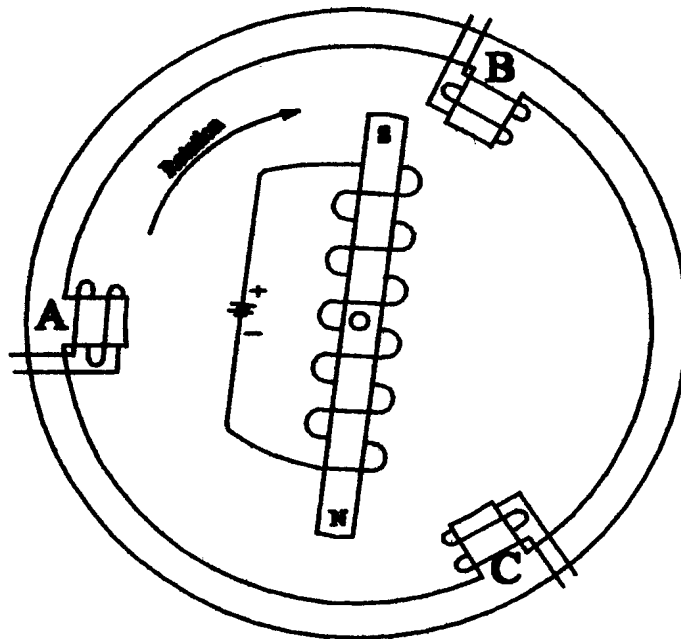


Simplified 3 Phase AC Generator


Field and Stator Windings

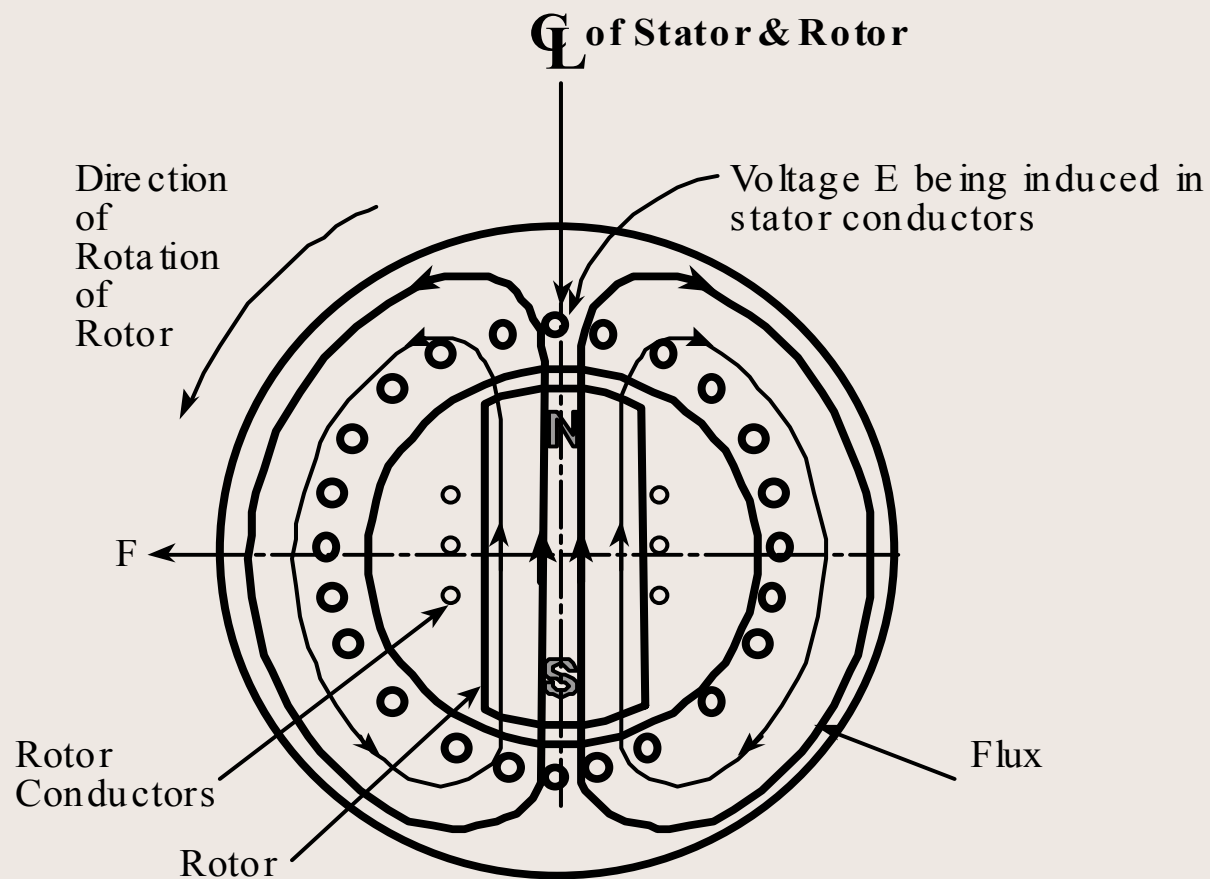

3 Phase Connections

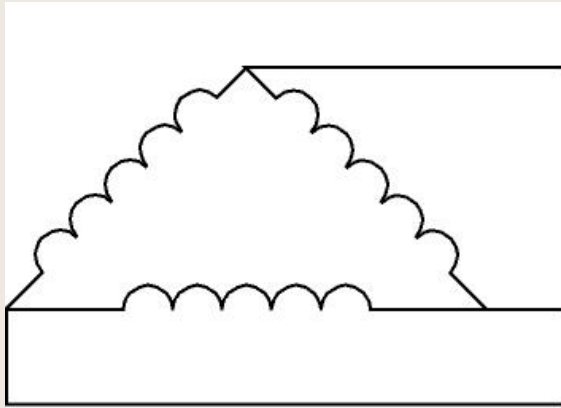


Delta

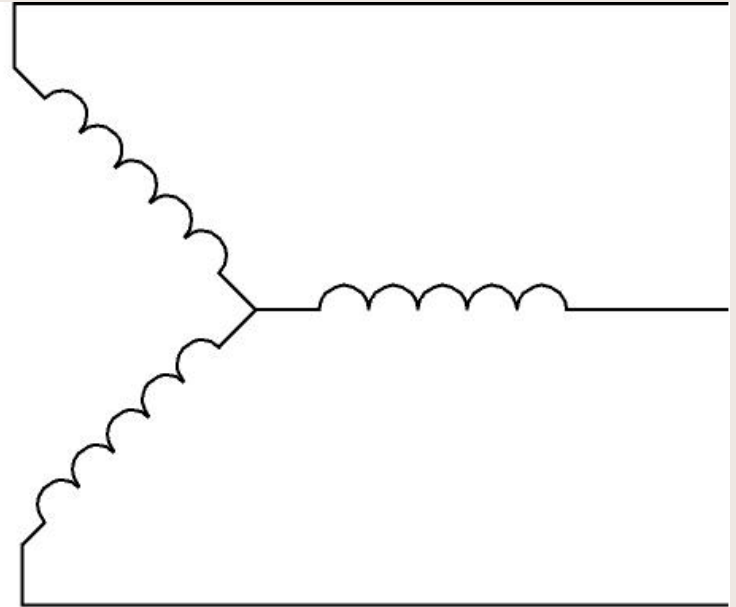

Star


Grounded Star

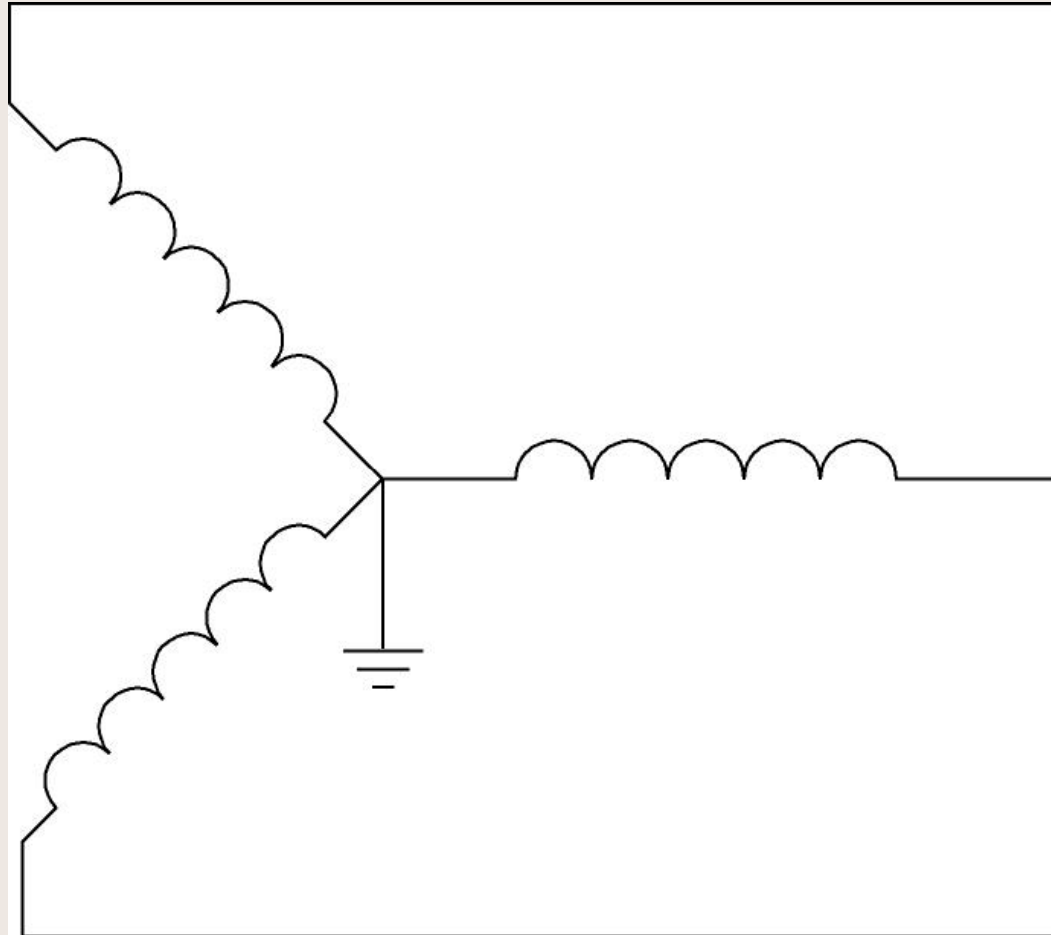

Magnetic Circuit Losses

- Hysteresis
- Eddy currents

Saturation Curve

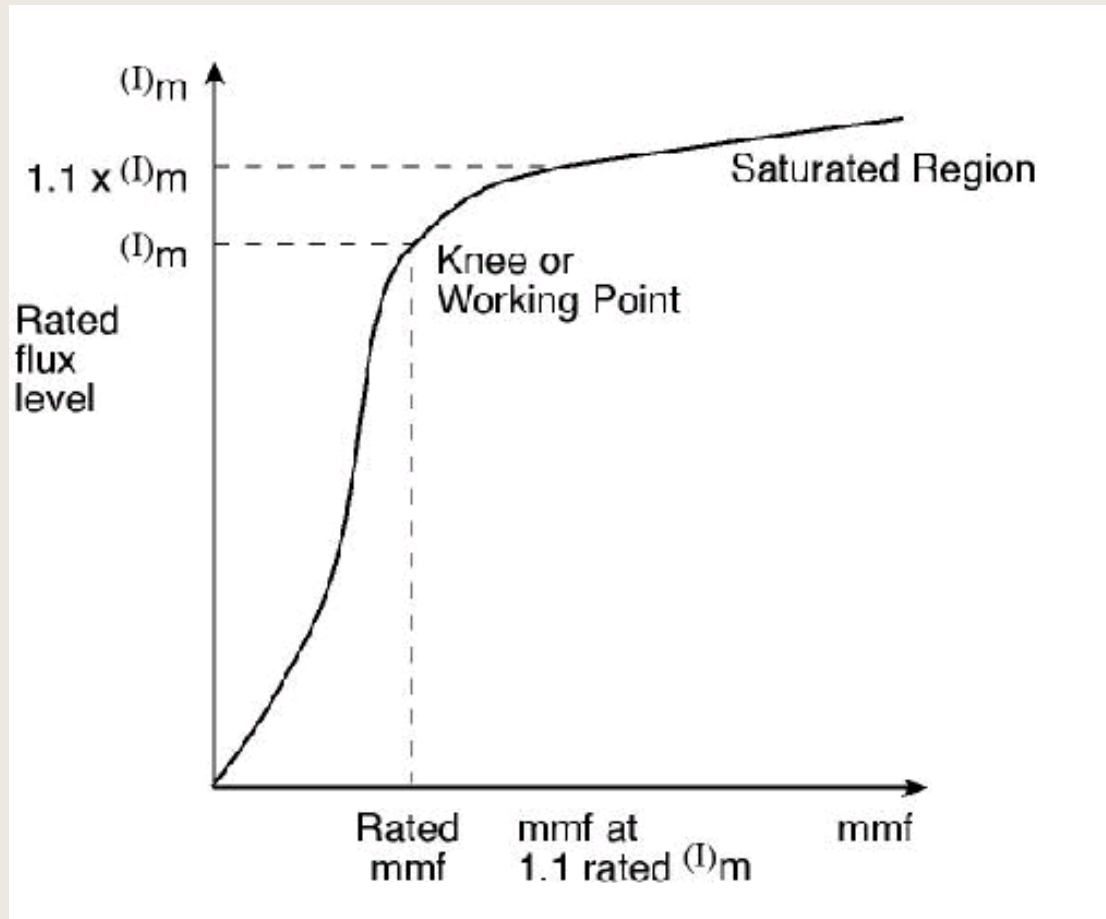

For you to do

Questions